

Question 1

A good problem statement for your automated turret system would accomplish the following (circle **all** that apply):

- (a) Allow for design trade space and open-ended solutions
- (b) Ensure the design looks exactly like the ones from the previous year
- (c) Include any constraints or clarifying data that scope the problem
- (d) Dictate the type of control algorithm required at the start of the project
- (e) Clarify both what the design will and won't do
- (f) Consider any external interactions and influences that could affect the design
- (g) Be very generic such that the objectives and design goals could be anything!

Question 2

The purpose of presenting thorough background research in an engineering report or publication is to (circle **all** that apply):

- (a) Justify the contribution by comparing it to existing projects
- (b) Increase the length of the document
- (c) Convince the reader that you are not “reinventing the wheel” (i.e. repeating an existing and fully documented project)
- (d) Demonstrate a understanding of the field
- (e) Background research serves no real purpose

Question 3

What is the purpose of the component shown in Fig. 1 (circle **one**)?



Figure 1: 50N06 MOSFET

- (a) Allow bidirectional control of a motor using logic level PWM and a direction pin
- (b) Acts as a switch and provides the required current to power to our motors
- (c) Look nice in your firing circuit
- (d) Prevent current from flowing back into an mBed

Question 4

What is the purpose of the components shown in Fig. 2 (circle **one**)?

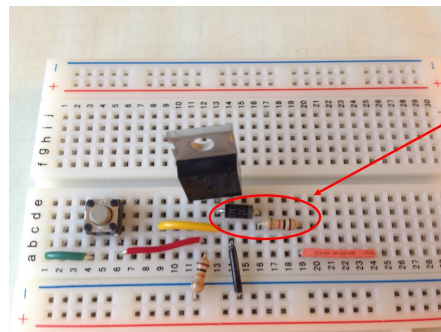


Figure 2: Manual Firing Circuit with important components highlighted and circled in red.

- (a) Ensures the voltage at the gate is set to 0V when the circuit is closed
- (b) Provide an adjustable, regulated voltage output
- (c) Look nice in your firing circuit
- (d) Allow a path for the inductive motor current to flow when the circuit is opened

Question 5

Why did we implement switches into the firing circuit prior to implementing the mbed (circle **all** that apply)?

- (a) To test a simplified version of the circuit prior to implementing a microcontroller
- (b) To inject a gratuitous discussion of switches into the course
- (c) To confirm proper circuit wiring prior to implementing a microcontroller
- (d) To avoid burning out Mbed I/O pins with improper circuit implementations

Question 6

Circle the pulldown resistor in Fig. 3.

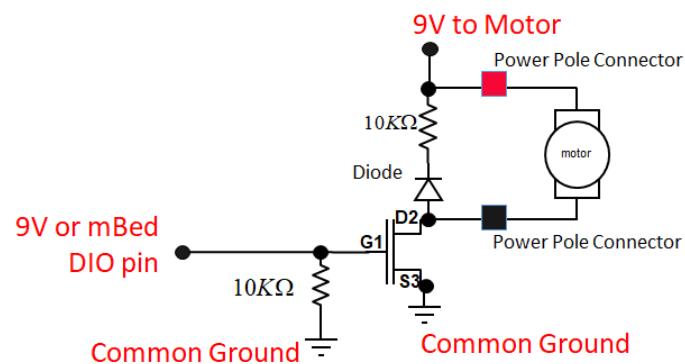


Figure 3: Single MOSFET-based firing circuit.

Question 7

Circle the snubber circuit in Fig. 4

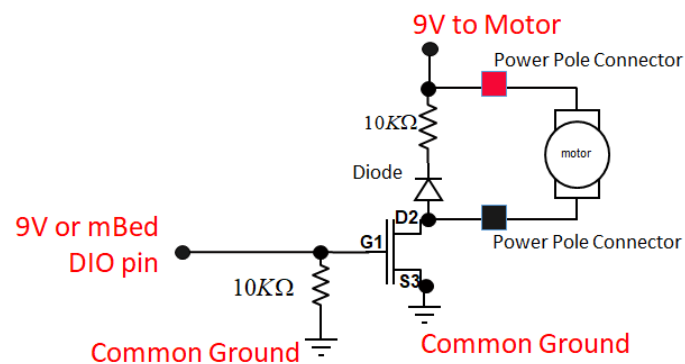


Figure 4: Single MOSFET-based firing circuit.

Question 8

What type of camera are we using for the computer vision subsystem of our project?

- (a) HD 720P 1.0MP Wide Angle Mini USB CCTV Camera
- (b) iCubie USB wecam
- (c) OV2710 high resolution micro USB camera
- (d) There is a camera in this project?

Question 9

What will happen when you set the mBed DIO pin to high in Fig. 5 (circle all that apply)?

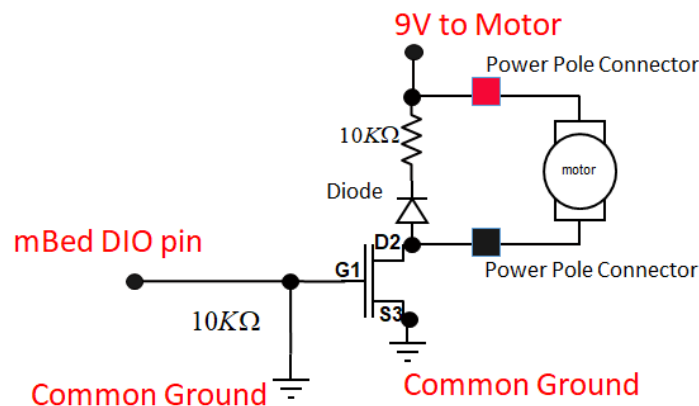


Figure 5: Single MOSFET-based firing circuit with a shorted-pulldown.

- (a) The motor will spin faster than normal
- (b) The motor will not spin at all
- (c) The switch and connected wires may get warm or even hot
- (d) The motor will spin slower than normal

Question 10

What is the purpose of computer vision in our EW309 project (circle all that apply)?

- (a) To process images using color thresholding
- (b) To find the centroid (center) of our desired target to eventually aim the turret
- (c) To process images using object properties
- (d) To estimate the conversion from linear units to pixels and vice versa